Lab3: Morse Code Decoder



National Chiao Tung University Chun-Jen Tsai 9/27/2016

Lab 3: Design a Morse Code Decoder


- In this lab, you will design a Morse code decoder module for a five-letter English word
 - The input is a 80-bit register that contains the Morse code of five English letters
 - The output is a 35-bit register of five 7-bit ASCII codes[†]
 - The circuit will be tested using a testbench with ISim, you do not have to synthesize the circuit for the Spartan 3 board
- □ You must demo to your TA during the Lab hours on Oct/11 that your circuit works with ISim

Morse Codes for English Alphabet

- □ In Morse code, there are "on" and "off" signals
 - A dot is one unit of "on"
 - A dash is three units of "on"
 - A space can be one, three, or seven units of "off"
- ☐ If we use 0 for "off" and 1 for "on", then:
 - A is 10111,
 B is 111010101,
 C is 11101011101,
 ..., etc.

International Morse Code

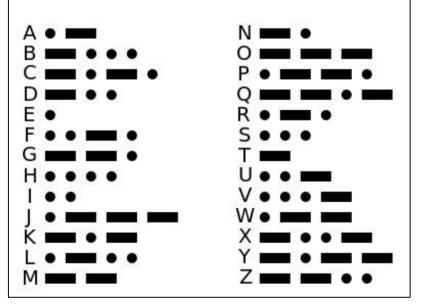- 1. The length of a dot is one unit.
- 2. A dash is three units.
- 3. The space between parts of the same letter is one unit.
- 4. The space between letters is three units.
- 5. The space between words is seven units.



■ The longest letters are composed of 13 bits (J, Q, and Y)

Binary Coding of Morse Code

□ The binary Morse codes of A~Z are listed below. Their hexadecimal codes are prefixed with zeros to 16 bits.

```
A 10111
                  (0x0017)
                              N 11101
                                                (0x001D)
                              0 11101110111
B 111010101
                  (0x01D5)
                                                (0x0777)
C 11101011101
                              P 10111011101
                                                (0 \times 05 DD)
                  (0x075D)
D 1110101
                  (0x0075)
                              0 1110111010111
                                                (0x1DD7)
E 1
                  (0x0001)
                              R 1011101
                                                (0x005D)
F 101011101
                  (0x015D)
                              S 10101
                                                (0x0015)
G 111011101
                  (0x01DD)
                              T 111
                                                (0x0007)
H 1010101
                  (0x0055)
                              U 1010111
                                                (0x0057)
I 101
                  (0x0005)
                              V 101010111
                                                (0x0157)
J 1011101110111 (0x1777)
                              W 101110111
                                                (0x0177)
K 111010111
                  (0x01D7)
                              X 11101010111
                                                (0x0757)
L 101110101
                  (0x0175)
                              Y 1110101110111
                                                (0x1D77)
                                                (0x0775)
M 1110111
                  (0x0077)
                              Z 11101110101
```

 \Box The ASCII codes of A~Z are 0x41~0x5A, respectively.

Decoder Module Specification

☐ The input/output ports of the multiplier is as follows:

```
module DecodeMorse(
    input clk,
    input enable,
    input reg [79:0] in_bits,
    output reg [34:0] out_text,
    output valid);
```

'clk' is the system clock,

'enable' raise it to '1' activates the decoding operation,

'in_bits' is the input Morse code bitstream,

'out_text' is the 7-bit ASCII codes of the output word,

'valid' will be raised to '1' when the output is valid


Decoding Behavior

- □ The input register, in_bits, has 80 bits because a five-letter Morse can have up to 80 bits: (13 bits of code + 3 zero bits) $\times 5 = 80$
- ☐ You can shift in_bits into a 16-bit register, say dec_reg, one bit per clock cycle until you see three zero bits at the most significant bits of in_bits, in which case dec_reg contains the binary Morse code of a letter
- □ The most challenging task in this lab is to design an efficient code conversion circuit to convert the binary Morse code to a 7-bit ASCII code

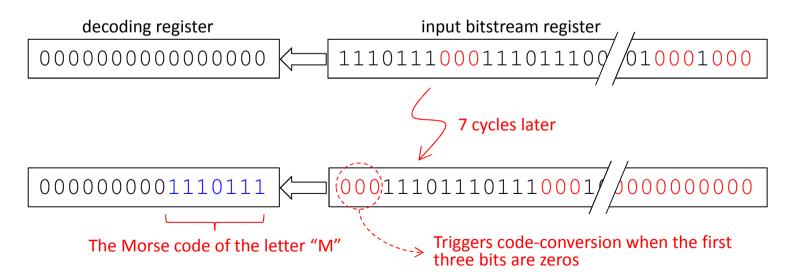Example of Decoding "MORSE"

☐ The five-letter word "MORSE" in binary Morse code has 46 bits:

☐ The decoding process involves shifting the input bitstream into a 16-bit decoding register:



Comments on Lab3

- ☐ The simplest way to do code conversion is to use a long list of if-then-else statements in Verilog

 > it should work, but not a good coding style
 - → it should work, but not a good coding style
- □ Please try to use the knowledge you have learned from Mano's book† to design a better way to do code conversion (*Hint: you may want to review Chapter 3*)